

DLD Project 2019 Combination Lock 10 % of Total Grade

Due 11:30 PM Tuesday Dec. 11 Through Sakai. Projects late will be accepted with 20% penalty. No projects accepted after 13 Dec.

Questions will only be answered in class from 12 noon until 1:20. No answers will be given out at other times. I will not respond to emailed questions by email. I will only give the answers during class sessions. No questions will be answered after 1:20 Friday 6 December. So finish your project early. Don't expect any help unless you come to class and ask your questions for all to hear.

Task:

Design an electronic combination lock state machine that will only open with your RUID. First convert your RUID to binary because you will need the least 12 significant bits to open the lock. Use a decimal to binary converter that can be found on Google.

Your design will require a 16 state, state machine in which 8 of the states will be good and 8 will be not used. List the 16 states in binary order starting with 0000 and ending with 1111.

Upon power up, the machine will automatically go to the start up state. Use the least four significant bits of your binary RUID as your starting point. Your next 8 bits will be your X input to the machine. Starting with the 5th bit (b_4), advance through the machine until you reach the 12th bit as follows: if your bit is a "0" then advance to the next binary state; but if your bit is a "1" then advance by skipping the next state and go to the state after that. Pick any unused state as your **lockout** state. All "bad states" (including the lockout state) will go to the lockout state upon $X=1$ or $X=0$. The machine will exit the lockout state by power off then on.

For example: if you are in state 1001 and your $X = 0$ go to 1010 but if $X = 1$ the go to 1011. Use this procedure for all 8 bits from bit 5 to 12. In your advancing when you reach 1111 wrap around to 0000 and then continue. Remember bit 5 is b_4 and the 12th bit is b_{11} .

There is one input, X, and two outputs: R (lights a red LED) and G (lights a green LED). The 12th bit will return you to the start state whether it is correct or not.

Each correct input bit will advance to the next expected state, any wrong input bit will send the machine to the lockout state and output R will = 1. When successfully starting at the right place and receiving bits 5 through 12 correctly, the machine will return to the start state and output G = 1 which will unlock the lock.

Note: After the user has successfully gained experience opening the lock, he can destroy the red LED to prevent an unauthorized user from employing the red LED to help break the lock combination. Assume that when powering up the machine automatically starts in your start state.

Deliverables:

- 1) Cover page with name, date, RUID, and RUID in binary.
- 2) State diagram with all 16 states including the start state, the 8 states that you are using and the 8 unused states.
- 3) State table showing the 16 states and $X=0$, $X=1$.
- 4) Excitation table for JK FF.
- 5) One 16 State transition table for J and K with $X=0$.
- 6) One 16 State transition table for J and K with $X=1$.
- 7) One 16 State transition table for the outputs R and G with $X=0$.
- 8) One 16 State transition table for the outputs R and G with $X=1$.
- 9) One each 5 variable K map for outputs R and G.
- 10) Eight, 5 variable K maps for q_3 , q_2 , q_1 , q_0 and X or you can do:
Sixteen, 4 variable K maps. Eight for J K $X=0$ and Eight for J K $X=1$.
- 11) Reduced equations for J_3 , J_2 , J_1 , J_0 and K_3 , K_2 , K_1 , K_0 .

12) One page discussion of your design, explain problems you had with this project and how you resolved them. Also how the project can be made better.

Minus 1 point for each missing item!